

# Operational Amplifiers and Transfer Functions



---

Changhai Wang

c.wang@hw.ac.uk
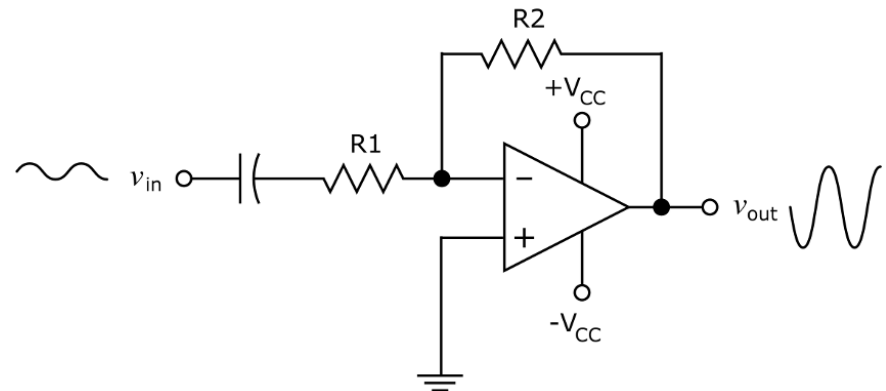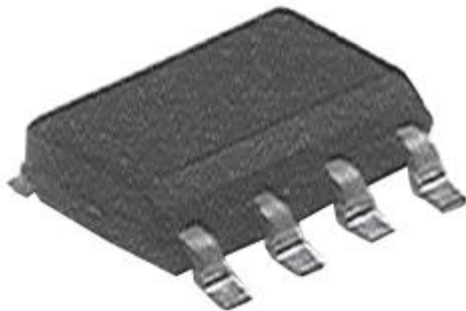
# Integrating Circuits and Operational Amplifiers


- In 1952, Geoffrey Dummer, a British electronics engineer, presented his idea for combining multiple circuit elements onto a single piece of semiconductor material with no connecting wires.
- In the summer of 1958, Jack Kilby, a newly employed engineer at Texas Instruments working alone in a lab (his colleagues were on vacation but he wasn't, as he did not yet have the right to a summer vacation) was able to build multiple circuit components out of a single, monolithic piece of germanium (a semiconductor material), and lay metal connectors in patterns on top of it.
- The most popular type of IC is the **operational amplifier**, nicknamed the **op amp**, which is designed to amplify a weak signal. An op amp contains several transistors, resistors, and capacitors, and offers more robust performance than a single transistor. An op amp can provide uniform amplification over a much wider range of frequencies (*bandwidth*) than a single-transistor amplifier.


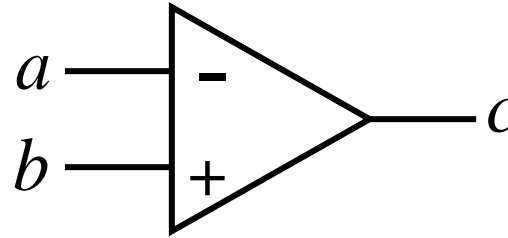
# Operational Amplifiers

An *operational amplifier* or *op amp* is a circuit that takes an input voltage and amplifies it.

An **ideal op amp**: an ideal model of an operational amplifier



$$V_a = V_b$$
$$I_a = 0 = I_b$$

If you would like to know what is inside an *op amp*, watch the following video


<https://www.youtube.com/watch?v=Q3RMFpGGcZM>, for example. Many other excellent explanations can be found on youtube.

However, in this course, we consider only with *ideal op amps*.

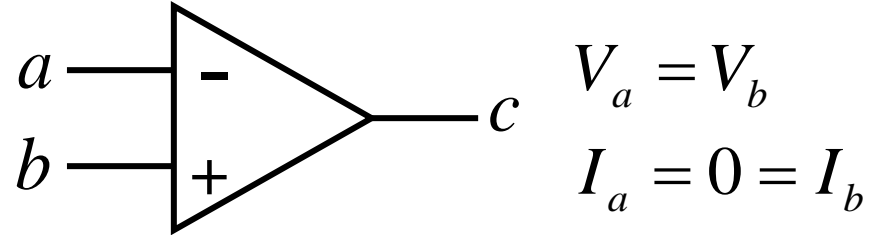
# Operational Amplifiers

An *operational amplifier* or *op amp* is a circuit that takes an input voltage and amplifies it.

An **ideal op amp**: an ideal model of an operational amplifier




## A noninverting amplifier

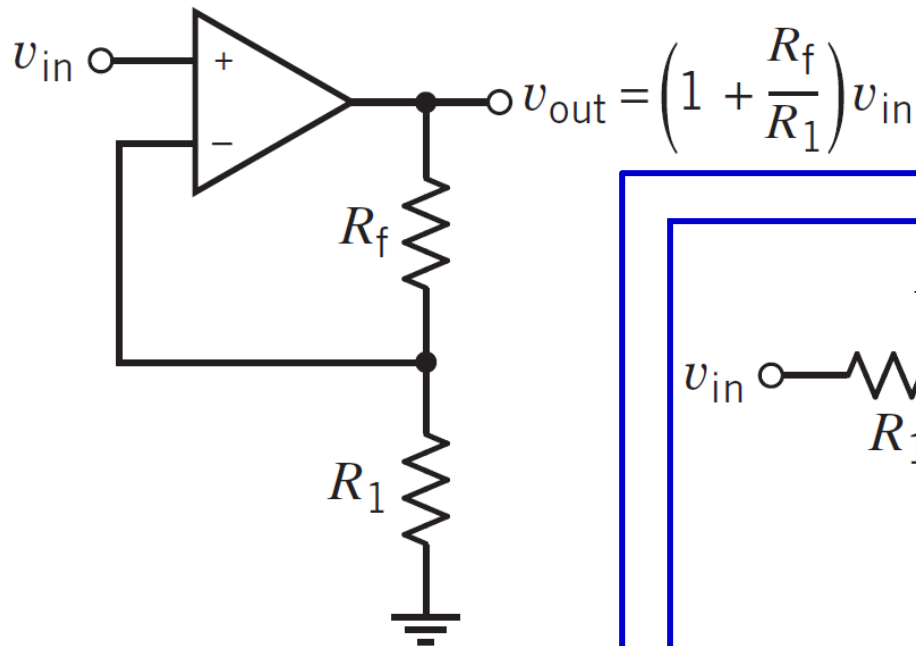



Use nodal analysis to study properties of these circuits

## An inverting amplifier

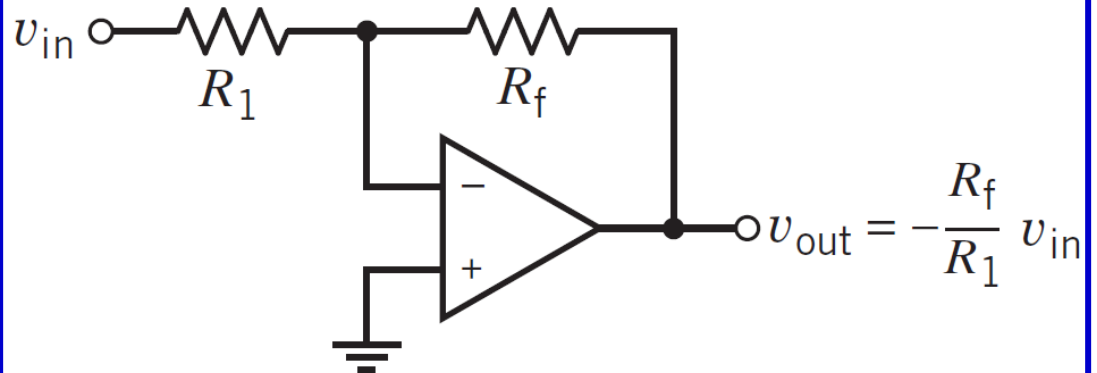

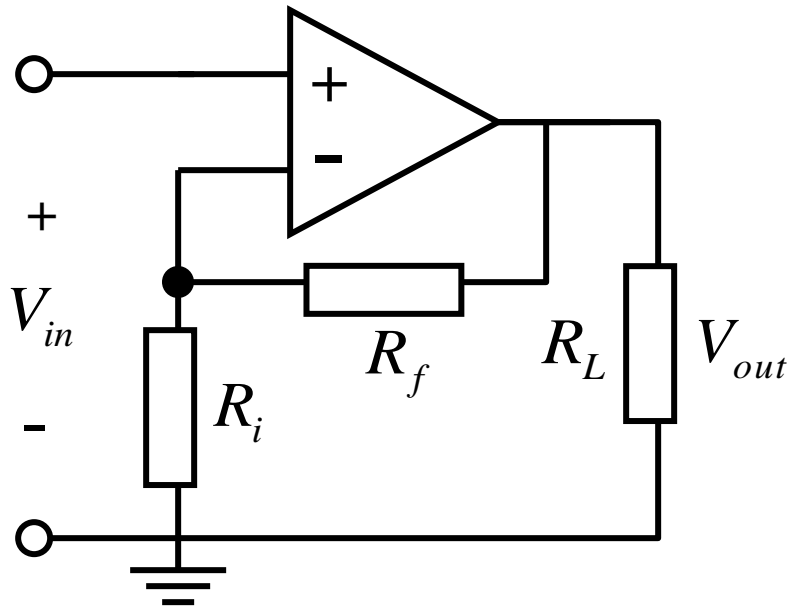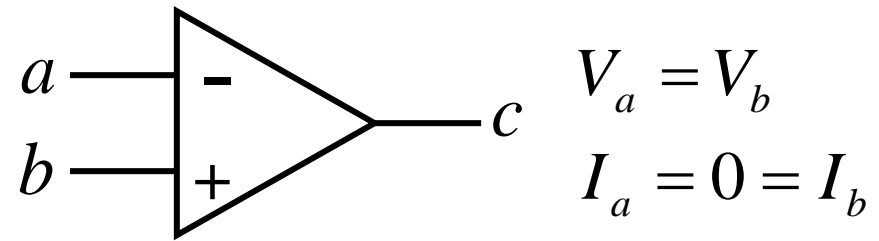
# Operational Amplifiers

Use nodal analysis to study properties of these circuits



A noninverting amplifier

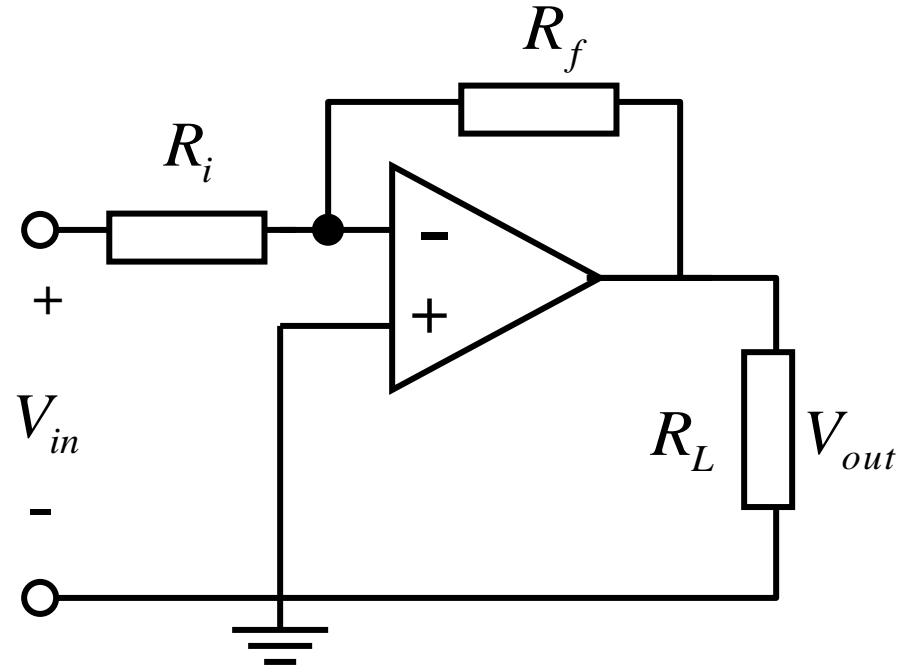
$$\frac{V_{in}}{R_i} = \frac{V_{out} - V_{in}}{R_f} \quad V_{out} = V_{in} \left( 1 + \frac{R_f}{R_i} \right)$$



An inverting amplifier

$$\frac{V_{in}}{R_i} = -\frac{V_{out}}{R_f} \quad V_{out} = -\frac{R_f}{R_i} V_{in}$$


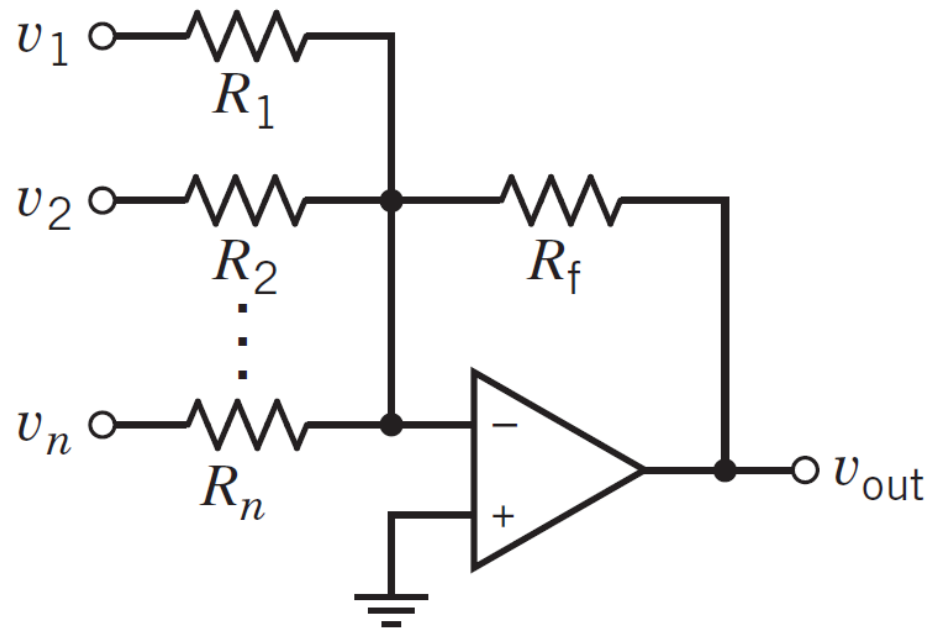
# Circuit Design with Operational Amplifiers



$$v_{out} = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots + \frac{R_f}{R_n} v_n\right)$$

Summing amplifier

# Summing Amplifier

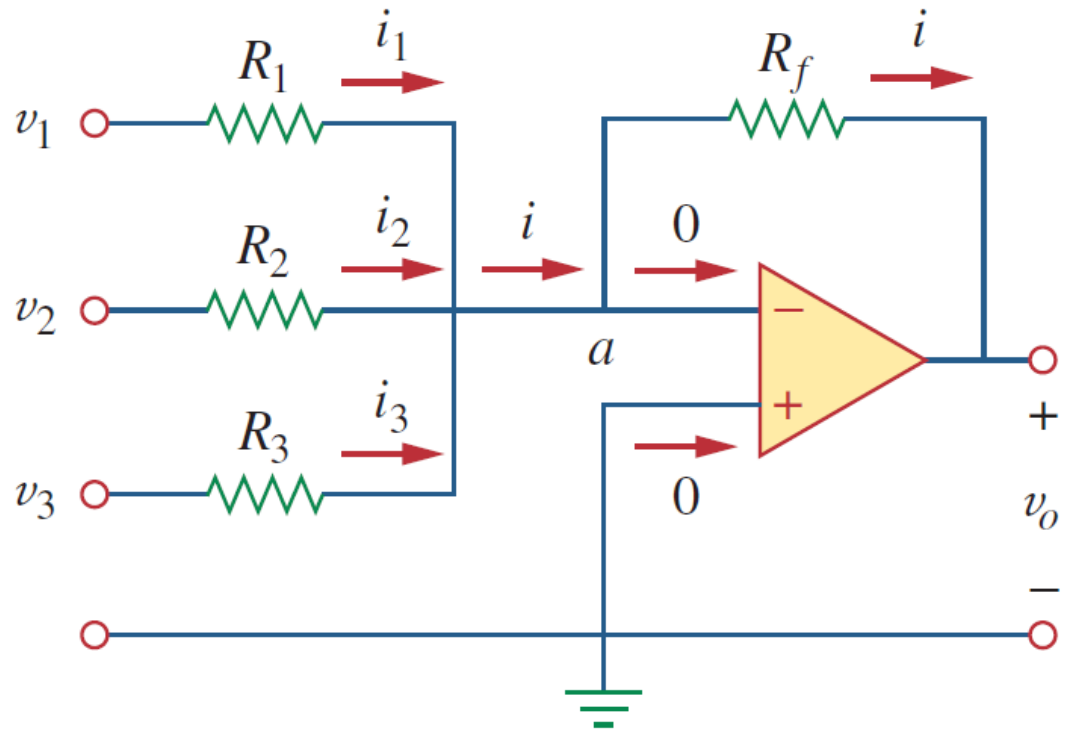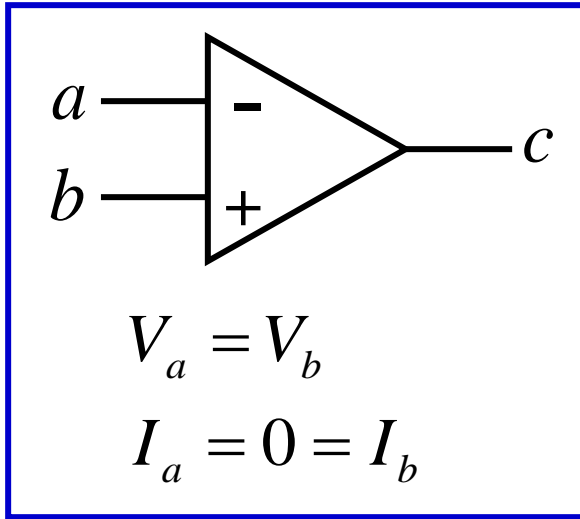

$$-\frac{v_o}{R_f} = i = i_1 + i_2 + i_3 = \frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3}$$

$$v_o = -\left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$

# Difference Amplifier

$$\frac{v_1 - v_a}{R_1} = \frac{v_a - v_o}{R_2}$$



$$v_o = \left( \frac{R_2}{R_1} + 1 \right) v_a - \frac{R_2}{R_1} v_1$$

$$\frac{v_2 - v_b}{R_1} = \frac{v_b - 0}{R_2}$$

$$v_b = \frac{R_4}{R_3 + R_4} v_2$$

$$v_a = v_b \Rightarrow v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} v_a - \frac{R_2}{R_1} v_1$$
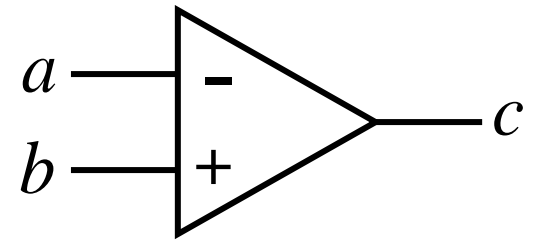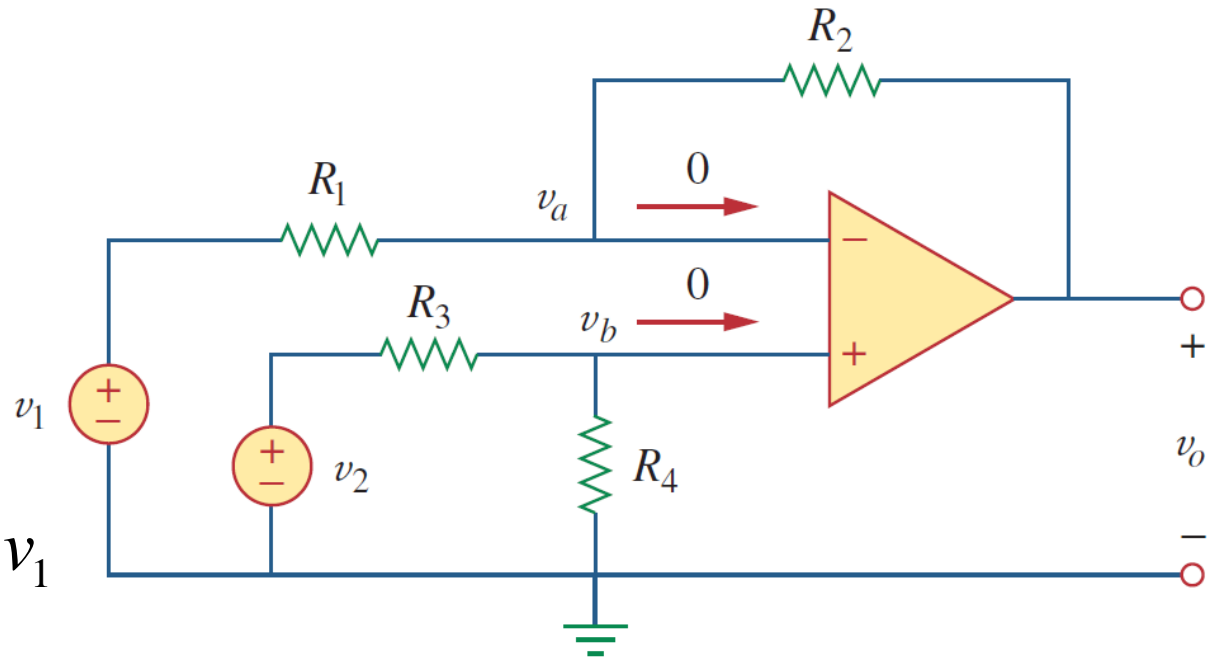
$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \Rightarrow v_o = \frac{R_2}{R_1} (v_2 - v_1)$$




$$V_a = V_b$$


$$I_a = 0 = I_b$$



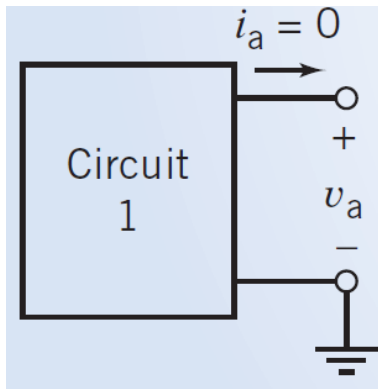
## An example: Preventing Loading Using a Voltage Follower



Circuit 2 is connected to Circuit 1.

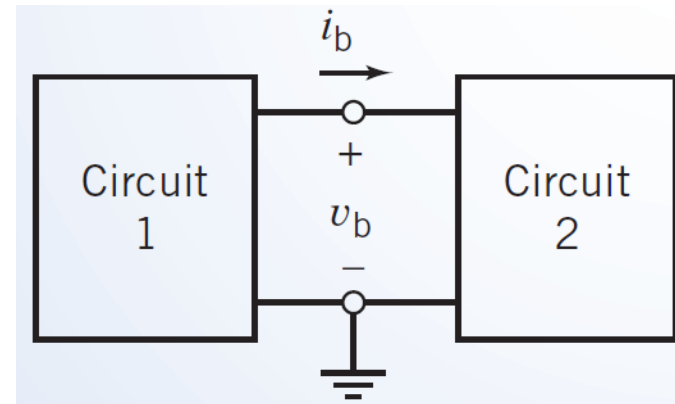


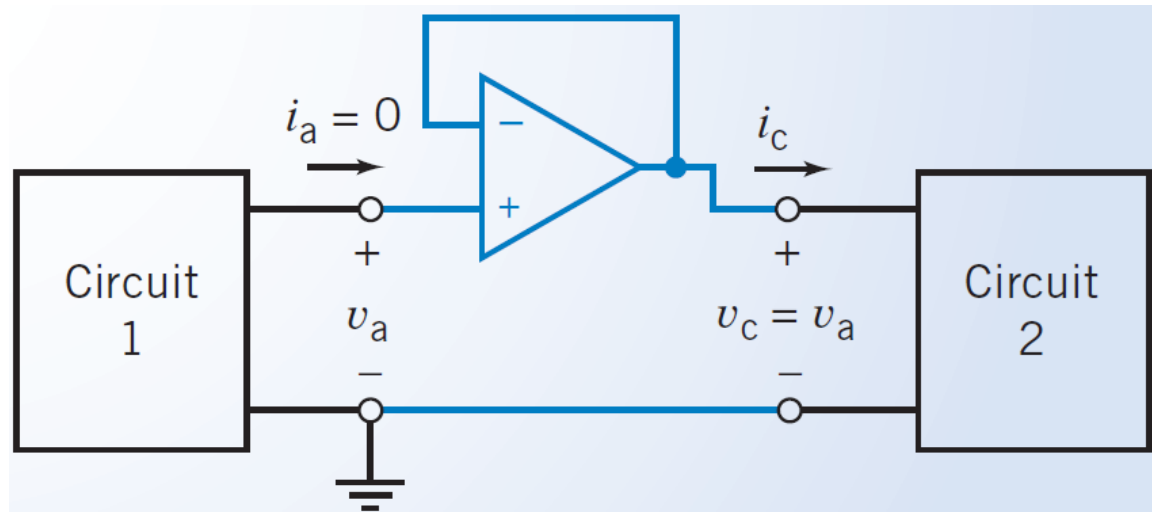The output of 1 is used as the input to 2. Unfortunately, connecting c2 to 1 can change the output of circuit 1. This is called loading.



The voltage follower copies voltage  $v_a$  from the output of circuit 1 to the input of circuit 2 without disturbing circuit 1.

# Op Amps in AC Circuits

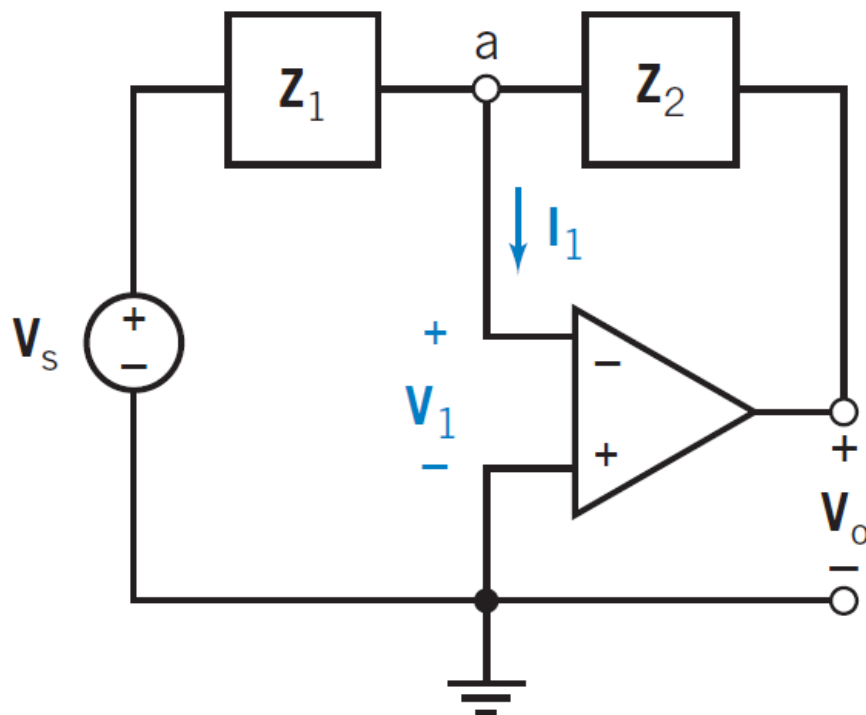

Let us use nodal analysis:

$$\frac{V_s - V_1}{Z_1} + \frac{V_o - V_1}{Z_2} = I_1$$

$$V_1 = 0 \quad I_1 = 0$$


$$\frac{V_s}{Z_1} + \frac{V_o}{Z_2} = 0$$

$$\frac{V_o}{V_s} = -\frac{Z_2}{Z_1}$$
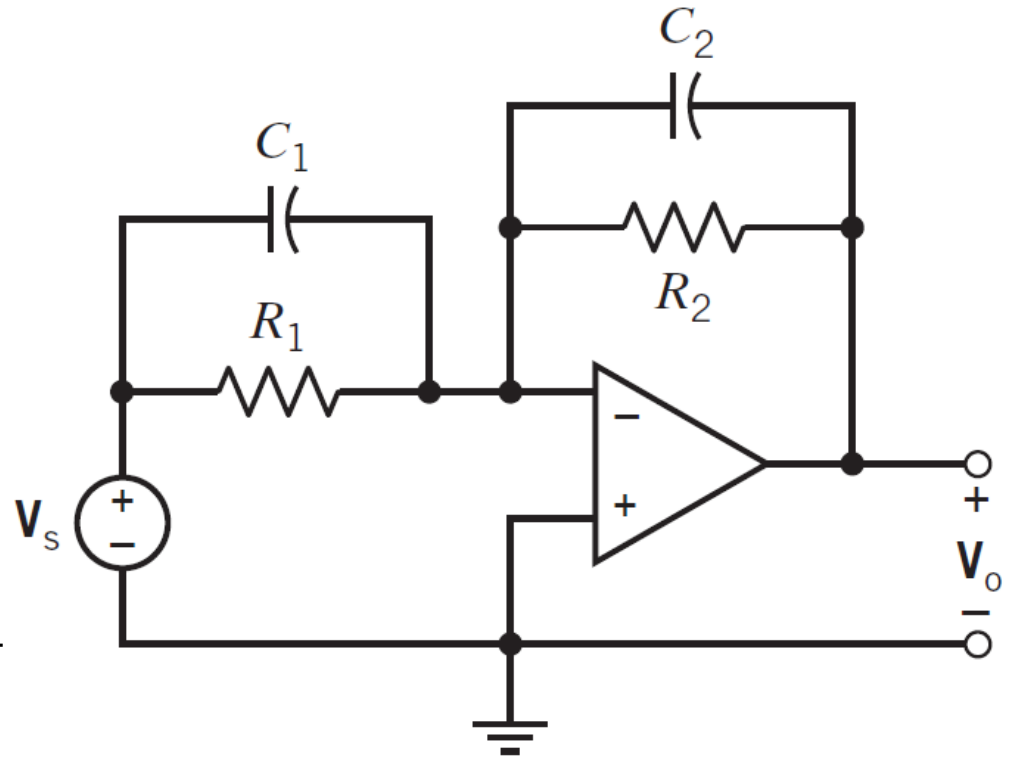
# Op Amps in AC Circuits

$$\frac{V_0}{V_s} = -\frac{Z_2}{Z_1}$$

$$Z = \frac{R/(sC)}{R + 1/sC} = \frac{R}{1 + sCR}$$





$$\frac{V_0}{V_s} = -\frac{Z_2}{Z_1} = -\frac{\frac{R_2}{1 + sC_2R_2}}{\frac{R_1}{1 + sC_1R_1}} = -\frac{R_2(1 + sC_1R_1)}{R_1(1 + sC_2R_2)}$$

# Transfer function 1

Determine the transfer function  $H(s) = I_o(s) / V_i(s)$ . Assume all initial conditions are zero.

**Solution:**

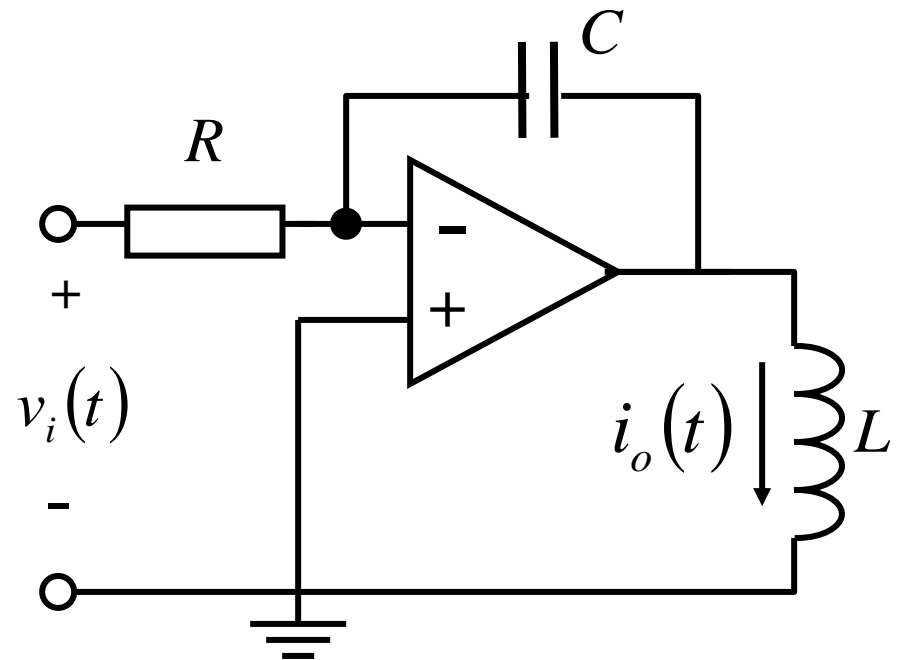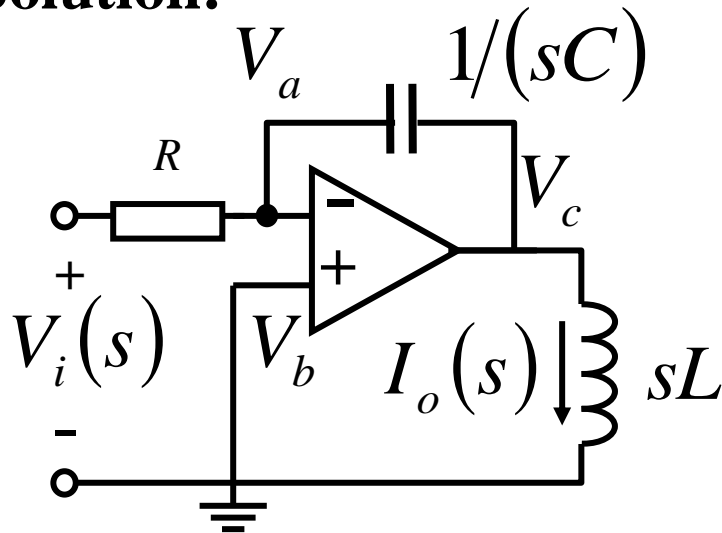

$$V_a = V_b = 0 \quad I_o = V_c / (sL)$$



$$\frac{V_a - V_i}{R} + \frac{V_a - V_c}{1/(sC)} = 0$$

$$H(s) = \frac{I_o(s)}{V_i(s)} = -\frac{1}{s^2 RCL}$$

# Transfer function 2

Determine the transfer function  $H(s) = V_o(s) / V_i(s)$ . Assume all initial conditions are zero.

**Solution:**

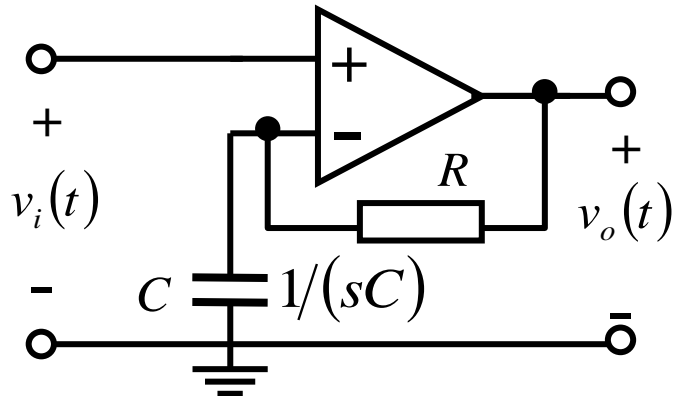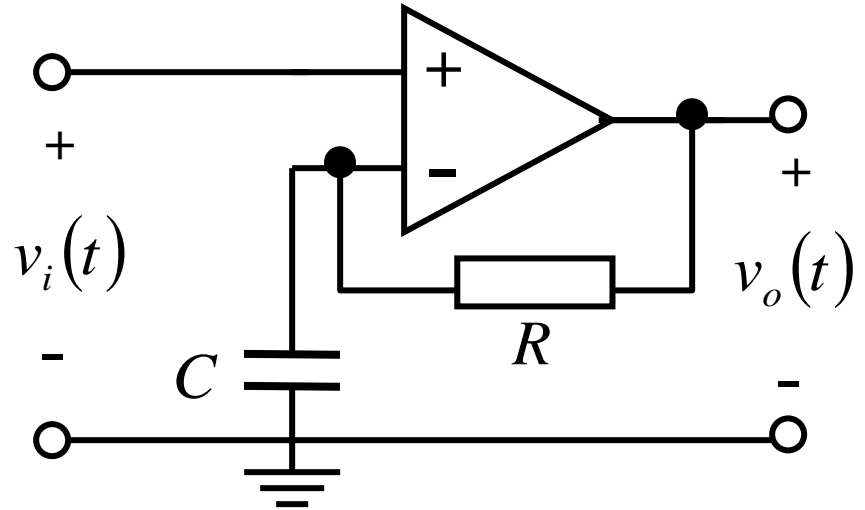

$$\frac{V_i - V_o}{R} + V_i(sC) = 0$$

$$V_o = V_i (1 + sRC)$$

$$H(s) = \frac{V_o}{V_i} = 1 + sRC$$